



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Automotive](#) > APP 1115

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Power-Supply Circuits](#) > APP 1115

Keywords: subscriber line interface card, SLIC, boost controller, transformer flyback topology, optocoupler, shunt voltage regulator, linear voltage regulator

APPLICATION NOTE 1115

Isolated SLIC supply

Jun 14, 2002

Abstract: This application note shows a power supply that generates three isolated voltages for SLICs. The isolated power supply uses a boost controller, the MAX668, with a transformer in flyback topology for -24V, and -72V outputs, and isolates the feedback signal with an optocoupler. A linear voltage regulator, the MAX8867, provides the 3.3V output.

A similar version of this article appeared in the September 24, 2001 issue of *EE Times* magazine.

Some subscriber line interface cards (SLICs) require power-supply voltages isolated from the local supply. The **Figure 1** circuit generates three such isolated voltages from a 5V input: +3.3V at 100mA, -24V at 100mA, and -72V at 25mA. It features a boost controller (U1) operating in a transformer flyback topology, and an optocoupler for isolating the feedback signal. To provide this feedback (from the -24V output to the boost controller) the optocoupler (U4) is driven by a shunt voltage regulator (U3) acting as an error amplifier.

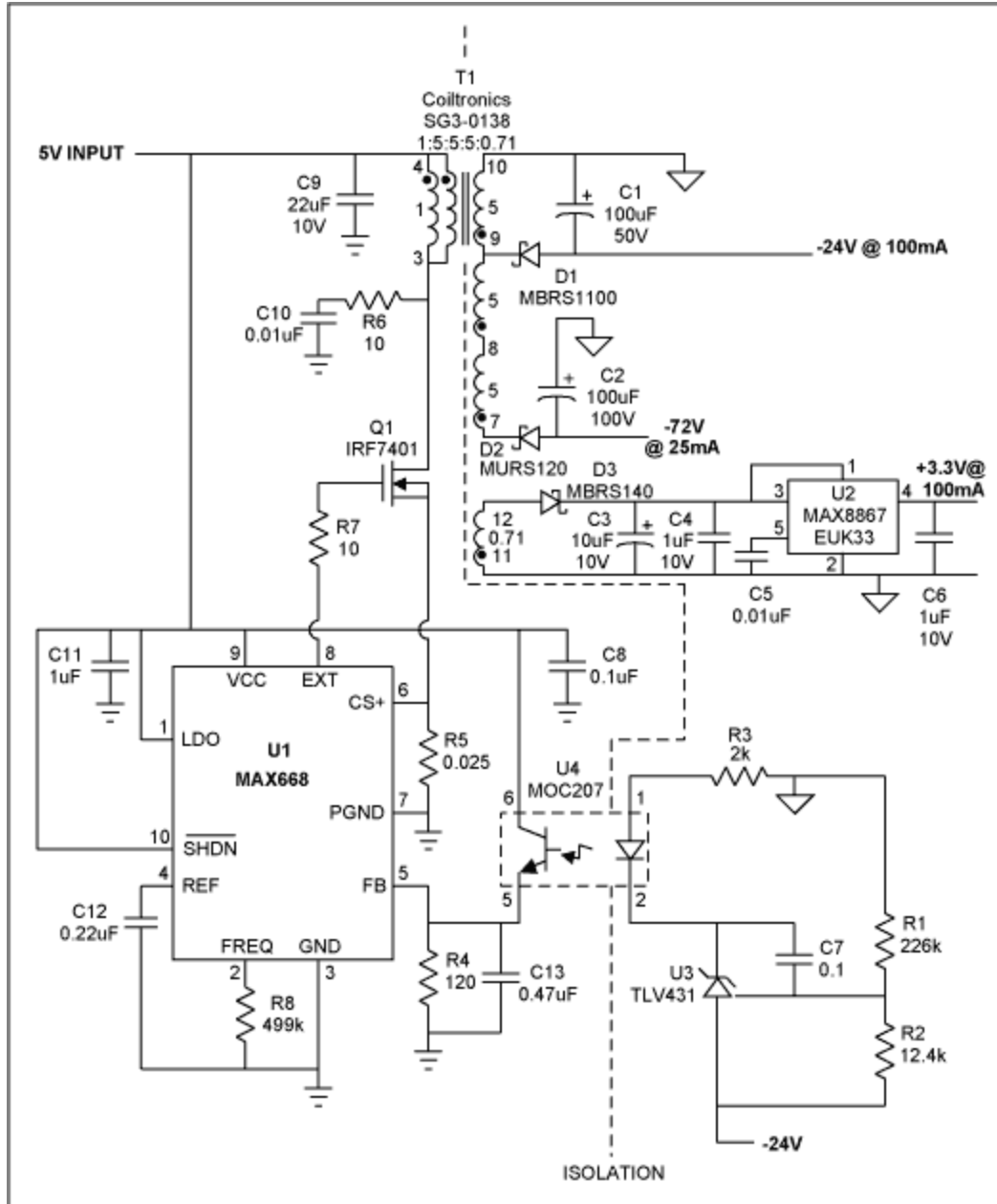


Figure 1. This SLIC power supply isolates the three outputs (+3.3V, -24V, and -72V) with a transformer, and isolates the feedback signal with an optocoupler.

The wide range of output voltages requires a custom transformer. Its core is a standard-geometry Coiltronics SG3-0138 with $A_L = 138\text{nH/T}^2$. The primary inductance is $6.8\mu\text{H}$, and the peak primary current is 4A. The primary-to-secondary turns ratio is 1:5, so for best efficiency the converter operates with a duty cycle near 50%. The unregulated -72V output is derived from the regulated -24V output via three identical secondary windings connected in series. Also available is a tap for a -48V output, and a low-voltage winding that drives a linear voltage regulator (U2) to provide the +3.3V output. The transformer's winding specs are:

Primary: 7T 28AWG bifilar

Secondary: 35T 32AWG
35T 32AWG
35T 32AWG
5T 32AWG

At maximum specified load with an input of 5.0V at 1.138A, the circuit yields 80% efficiency while delivering +3.28V at 103.9mA, -24.0V at 100mA, and -73.2V at 25.2mA.

V _{IN} (V)	I _{in} (A)	V _o (V)	I _o (mA)	V _o (V)	I _o (mA)	V _o (V)	I _o (mA)	Eff. (%)
4.50	1.27	24.01	100.2	73.2	25.2	3.28	103.9	80.3
5.01	1.138	24.01	100.2	73.2	25.2	3.28	103.9	80.5
5.50	1.038	24.01	100.2	73.2	25.2	3.28	103.9	80.4

Notes:

1. T1 is wound on a standard geometry core with 138nH/T².
Primary inductance is 6.7μH.
Primary is 7 turns of #28 bifilar.
Tapped secondary is three layers of 35 turns each of #32 per tap.
Low voltage secondary is 5 turns of #32.

Related Parts

MAX668	1.8V to 28V Input, PWM Step-Up Controllers in μMAX	Free Samples
MAX8867	Low-Noise, Low-Dropout, 150mA Linear Regulators in SOT23	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>
For Samples: <http://www.maximintegrated.com/samples>
Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1115: <http://www.maximintegrated.com/an1115>
APPLICATION NOTE 1115, AN1115, AN 1115, APP1115, Appnote1115, Appnote 1115
Copyright © by Maxim Integrated Products
Additional Legal Notices: <http://www.maximintegrated.com/legal>